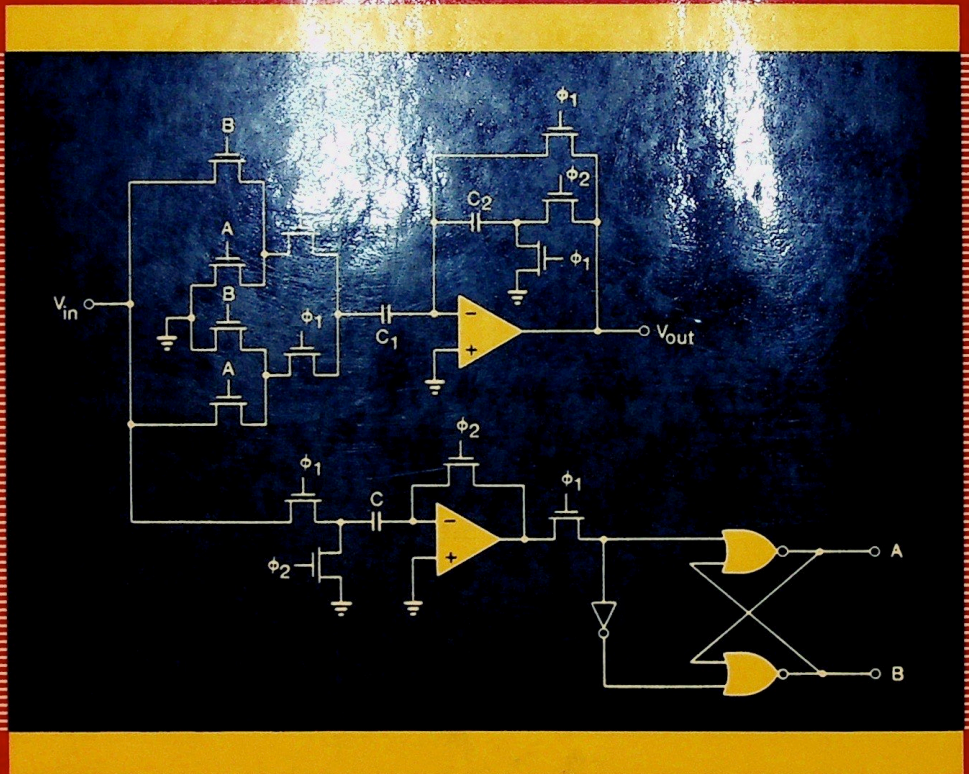


Analog MOS Integrated Circuits

FOR SIGNAL PROCESSING



ROUBIK GREGORIAN

GABOR C. TEMES

A volume in the Wiley Series on Filters: Design, Manufacturing and Applications; Robert A. Johnson & George Szentirmai, Editors

This book is both a reference for industry and a textbook. It is a practical and practical design guide for analog MOS integrated circuits. *MOS Integrated Circuits for Signal Processing* both explains the underlying principles and shows professional engineers and advanced students how to design them. Only a minimum of mathematics, electronics, and semiconductor physics are required. *MOS Integrated Circuits* provides a streamlined design that reflects the state of the art in both public and private courses given for many years. The theory is not restricted to theoretical design; a number of design examples are available to compare the book focuses on the most widely tested one.

The first three chapters provide a basic description of the circuits, and the necessary background mathematics (Laplace transforms) and device physics are presented. The rest of the book is devoted to the analysis and design of circuits as switches, analog-to-digital converters, and oscillators, and also discusses the problems encountered in the design and provides solutions, and examples of actual designs. To enhance reference, *Analog Circuits* includes numerical design and step-by-step procedures and exercises that test the reader's understanding of the book.

WILEY SERIES ON FILTERS: Design, Manufacturing, and Applications

Editors: Robert A. Johnson and George Szentirmai

Mechanical Filters in Electronics

Robert A. Johnson

LC-Filters: Design, Testing, and Manufacturing

Erich Christian

Analog MOS Integrated Circuits for Signal Processing

Roubik Gregorian and Gabor C. Temes

ANALOG MOS INTEGRATED CIRCUITS FOR SIGNAL PROCESSING

ROUBIK GREGORIAN

Sierra Semiconductor
San Jose, California

GABOR C. TEMES

Department of Electrical Engineering
University of California, Los Angeles

A Wiley-Interscience Publication

JOHN WILEY & SONS

New York Chichester Brisbane Toronto Singapore

Copyright © 1986 by John Wiley & Sons, Inc.

All rights reserved. Published simultaneously in Canada.

Reproduction or translation of any part of this work beyond that permitted by Section 107 or 108 of the 1976 United States Copyright Act without the permission of the copyright owner is unlawful. Requests for permission or further information should be addressed to the Permissions Department, John Wiley & Sons, Inc.

Library of Congress Cataloging in Publication Data:

Gregorian, Roubik.

Analog MOS integrated circuits for signal processing.

(Wiley series on filters)

"A Wiley-Interscience publication."

Includes bibliographies and index.

1. Switched capacitor circuits. 2. Linear integrated circuits. 3. Metal oxide semiconductors. I. Temes, Gabor C., 1929- II. Title. III. Series.
TK7868.S88G74 1986 621.381'73 85-31493
ISBN 0-471-09797-7

Printed in the United States of America

10 9 8 7 6

CONTENTS

Chapter One. Introduction	1
1.1. The Use of Analog MOS Integrated Circuits for Signal Processing	1
1.2. Comparison of Analog MOS Signal Processors with Other Implementations	6
1.3. Examples of Analog MOS Signal Processing Circuits and Systems	13
Problems	15
References	18
Chapter Two. Transformation Methods	19
2.1. Analog, Digital, and Sampled-Analog Signals and Systems	19
2.2. The Laplace Transformation	24
2.3. The Fourier Transformation	29
2.4. Sampling and the z-Transform	31
2.5. The Spectra of Sampled-Data Signals	39
2.6. The Design of Sampled-Data Filters from Continuous-Time Models	43
Problems	60
References	62
Chapter Three. MOS Devices as Circuit Elements	64
3.1. Semiconductors	64
3.2. The MOS Transistor	68
3.3. MOS Transistor Types; Body Effect	75
3.4. Small-Signal Operation and Equivalent Circuit of MOSFETs	78
3.5. MOS Capacitors	86
3.6. The MOS Switch	93
3.7. Noise in MOSFETs	96
3.8. Analog MOS Technology	99
Problems	118
References	120

Chapter Four. MOS Operational Amplifiers

121

- 4.1. Operational Amplifiers 121
- 4.2. Bias Circuits in MOS Technology 126
- 4.3. MOS Gain Stages 133
- 4.4. MOS Source Followers and Output Buffers 141
- 4.5. MOS Differential Amplifiers 146
- 4.6. The Frequency Response of MOS Amplifier Stages 156
- 4.7. Uncompensated CMOS Operational Amplifiers 168
- 4.8. Stability Theory and Compensation of CMOS Amplifiers 172
- 4.9. Frequency Response, Transient Response, and Slew Rate of the Compensated CMOS Op-Amp 182
- 4.10. Noise Performance of CMOS Amplifiers 186
- 4.11. An Enhancement-Mode NMOS Op-Amp 189
- 4.12. NMOS Op-Amps with Depletion Loads 196
- 4.13. The Noise Performance of NMOS Op-Amps 206
- 4.14. Practical Considerations in MOS Op-Amp Design 208
- 4.15. Op-Amp Design Techniques and Examples 222
- 4.16. High-Performance CMOS Op-Amps 246
 - Problems 259
 - References 264

Chapter Five. Switched-Capacitor Filters

265

- 5.1. Integrated Filters 265
- 5.2. Switched-Capacitor Integrators 270
- 5.3. Stray-Insensitive Integrators 277
- 5.4. Second-Order Sections; Cascade Filter Design 280
- 5.5. Switched-Capacitor Ladder Filters 296
- 5.6. The Scaling of Switched-Capacitor Filters 339
- 5.7. Design Examples 349
- 5.8. Switched-Capacitor N -Path Filters 363
- 5.9. Integrated Active-RC Filters Using MOSFET Resistors 387
 - Problems 404
 - References 409

Chapter Six. Nonfiltering Applications of Switched-Capacitor Circuits

411

- 6.1. Switched-Capacitor Gain Stages 412
- 6.2. Programmable Capacitor Arrays: Digital-to-Analog and Analog-to-Digital Converters 417
- 6.3. MOS Comparators 425
- 6.4. Modulators, Rectifiers, and Detectors 437

- 6.5. Switched-Capacitor Oscillators 445
- Problems 455
- References 460

***Chapter Seven. Nonideal Effects in Switched-Capacitor Circuits* 462**

- 7.1. Nonideal Effects in the Switches 462
- 7.2. Capacitance Inaccuracies 474
- 7.3. Nonideal Op-Amp Circuit Effects 483
- 7.4. Noise Generated in Switched-Capacitor Circuits 500
- 7.5. Layout Considerations in Switched-Capacitor Circuits 513
- Problems 524
- References 528

***Chapter Eight. System Considerations and Applications* 530**

- 8.1. Prefiltering Requirements for Switched-Capacitor Filters 530
- 8.2. Postfiltering for Switched-Capacitor Filters 539
- 8.3. The Application of Switched-Capacitor Circuits in Digital Voice Transmission Systems 545
- 8.4. The Application of Switched-Capacitor Circuits in Data Modems 561
- 8.5. The Application of Switched-Capacitor Filters in Tone Receivers 564
- 8.6. Programmable Switched-Capacitor Filters 571
- 8.7. The Application of Switched-Capacitor Circuits in Speech Processing 576
- Problems 589
- References 591

***Index* 593**

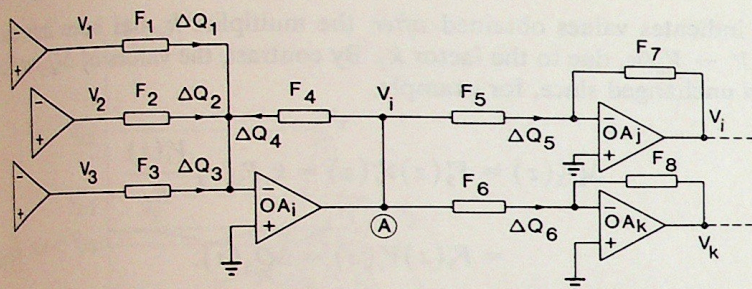


FIGURE 5.40. SC filter section.

For very narrow-band bandpass filters (say, with relative bandwidths of 1% or less) none of the design techniques described in this chapter are very effective, since they result in circuits which are too sensitive to finite op-amp gain effects, strays, and element-value variations. Then, design based on the *N-path filter concept* may be used. This concept, and the corresponding design techniques, are discussed in Section 5.8.

5.6. THE SCALING OF SWITCHED-CAPACITOR FILTERS^{19,36}

The actual performance of an SCF can be improved, and the area which it occupies on its silicon chip reduced, by scaling operations. To understand how such operations can be carried out, consider a segment of an SCF containing the i th op-amp OA_i and all branches connected to it. This is schematically illustrated in Fig. 5.40, in which the coupling branches may contain capacitors and switches in any arrangement. Each coupling branch in a stray-insensitive SCF is connected between an op-amp output and a virtual ground; each can be described by a transfer function $F_k(z) = \Delta Q_k(z)/V_i(z)$. Here, $\Delta Q_k(z)$ is the z -domain representation of the charge-per-clock-period sequence $q_k(nT)$ at the input of the branch.

Now let all branches connected to the *output* terminal of OA_i be modified such that their $\Delta Q/V$ transfer functions (F_4, F_5, F_6) are multiplied by a positive real constant factor k_i . This can be achieved simply by multiplying all capacitors in these branches by k_i , since (for given voltages connected across these branches) their charges are proportional to these capacitances.

Since the input branches and their voltages were left unchanged, the charge flowing in the feedback branch

$$\Delta Q_4(z) = -\Delta Q_1(z) - \Delta Q_2(z) - \Delta Q_3(z) \quad (5.93)$$

remains at its original value. The output voltage of OA_i (assuming ideal op-amps) thus becomes $V'_i(z) = \Delta Q_4(z)/[k_i F_4(z)] = V_i(z)/k_i$, where the

340 SWITCHED-CAPACITOR FILTERS

prime indicates values obtained *after* the multiplier k_i has been introduced. Thus, $V_i \rightarrow V_i/k_i$ due to the factor k_i . By contrast, the values of ΔQ_5 and ΔQ_6 remain unchanged since, for example,

$$\begin{aligned}\Delta Q'_5(z) &= F'_5(z)V'_i(z) = k_i F_5(z) \frac{V_i(z)}{k_i} \\ &= F_5(z)V_i(z) = \Delta Q_5(z).\end{aligned}\quad (5.94)$$

In conclusion, multiplying all capacitors which are connected (or switched) to the output terminal of the i th op-amp OA_i changes its output voltage V_i to V_i/k_i , while leaving all charges flowing from (and to) OA_i to (and from) the rest of the circuit unchanged. Thus, by this operation we can increase or decrease V_i by a constant scale factor without affecting any other voltages or charges in the SCF.

The described scaling operation is useful in improving the dynamic range of SC circuits. As defined in Section 4.1 of Chapter 4, the dynamic range is $20 \log_{10} (v_{in, \max}/v_{in, \min})$. Here, $v_{in, \max}$ is the maximum input signal which the SCF can handle without excessive nonlinear distortion; in an SCF, $v_{in, \max}$ is usually limited by the saturation of the op-amps. The minimum useful input signal $v_{in, \min}$ is the smallest value for which the SCF output voltage v_{out} can be distinguished from the output noise $v_{n, out}$.

In the following discussions it will be assumed that the dynamic range of the SCF is to be optimized using scaling. Consider the SC circuit schematically illustrated in Fig. 5.41. Let the amplitude of the largest output signal which the op-amps in the filter (assumed, for simplicity, to be identical) can handle be $V_{\max}$. Also, let the passband gain of the filter be A_p . Since v_{out} (produced by the output op-amp OA_n) is at most $V_{\max}$, we have

$$v_{in, \max} \leq V_{\max}/A_p. \quad (5.95)$$

Let the frequency responses of all op-amp outputs $V_1, V_2, \dots, V_i, \dots, V_n$ be as shown in Fig. 5.42, where a fifth-order low-pass filter is assumed. Then, as the amplitude of v_{in} is increased from a small value to $V_{\max}/A_p$ at a frequency near ω_2 (the peak frequency of V_2), OA_2 will saturate before OA_5 does since

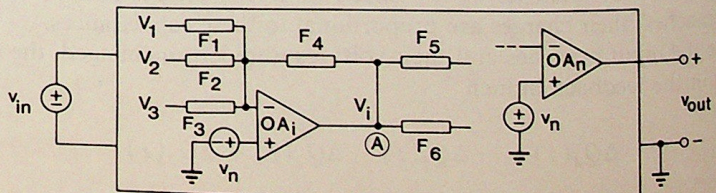


FIGURE 5.41. SC filter with noisy internal op-amp.

***More from the Wiley Series on Filters: Design,
Manufacturing and Applications...***

LC FILTERS

Design, Testing and Manufacturing

Erich Christian

This practical text addresses designers who have to carry out their task from given specifications, all the way to the construction of the unit and the subsequent job of assisting in its manufacture. Because modern filter design is both a science and an art, the book bridges the gap between theoretical methods, which are mostly mathematical, and the possible application of computer programs which are used for implementing the designs. To this end, virtually all numerical examples in the text are demonstrated in the form of computer-aided solutions with available programs.

1983 (0 471 09053-0) 242 pp.

MECHANICAL FILTERS IN ELECTRONICS

Robert A. Johnson

The first comprehensive book ever written on the subject describes the design, manufacture and use of mechanical filters to practicing engineers. There is enough theory developed in the book to enable the person who is new to mechanical filters to understand how they work, as well as how they are manufactured, specified, tested and used. The book provides experienced engineers in the field with a considerable amount of new and hard-to-find information, including material on equivalent mass equations and coupling wire equivalent circuits.

1983 (0 471 08919-2) 379 pp.

WILEY-INTERSCIENCE

a division of JOHN WILEY & SONS, Inc.

605 Third Avenue, New York, N.Y. 10158-0012

New York • Chichester • Brisbane • Toronto • Singapore

ISBN 0 471-09797-7



X00367FAS7

Analog MOS Integrated Circuits

Used - Good

H - 111588278

(2303)