

contents

preface v

chapter 1 Introduction and Background 1

- 1.1 Analog Integrated Circuit Design 2
- 1.2 Notation, Symbolology, and Terminology 9
- 1.3 Analog Signal Processing 14
- 1.4 Example of Analog Circuit Design 17
- 1.5 Summary 22
 - Problems* 26
 - References* 28

chapter 2 CMOS Technology 29

- 2.1 Basic MOS Semiconductor Fabrication Processes 31
- 2.2 PN Junction 38
- 2.3 MOS Transistor 48
- 2.4 Passive Components 58
- 2.5 Other Considerations of CMOS Technology 66
- 2.6 Geometrical Considerations of Integrated Circuits 76
- 2.7 Summary 86
 - Problems* 87
 - References* 92

chapter 3 CMOS Analog Circuit Modeling 95

- 3.1 Simple MOS Large-Signal Model 96
- 3.2 Other MOS Large-Signal Model Parameters 103
- 3.3 Small-Signal Model for the MOS Transistor 114
- 3.4 Second-Order Model Effects 119
- 3.5 Subthreshold MOS Model 124
- 3.6 Computer and Calculator Simulation of MOS Circuits 128
- 3.7 Summary 145
 - Problems* 146
 - References* 150

xi

chapter 4 CMOS Device Characterization 153	
4.1 Geometrical Aspects of Characterization 154	
4.2 Characterization of the Simple Transistor Model 155	
4.3 Transistor Characterization for the Extended Model 168	
4.4 $1/f$ Noise 172	
4.5 Characterization of Other Active Components 174	
4.6 Characterization of Resistive Components 177	
4.7 Characterization of Capacitance 184	
4.8 Summary 190	
Problems 190	
References 195	
chapter 5 Analog CMOS Subcircuits 197	
5.1 MOS Switch 198	
5.2 Active Resistors/Loads 211	
5.3 Current Sinks and Sources 219	
5.4 Current Mirrors and Current Amplifiers 227	
5.5 Current and Voltage References 240	
5.6 Summary 251	
Problems 252	
References 256	
chapter 6 CMOS Amplifiers 257	
6.1 Inverters 258	
6.2 Differential Amplifiers 273	
6.3 Cascode Amplifier 287	
6.4 Output Stages 299	
6.5 High Gain Amplifier Architectures 308	
6.6 Summary 313	
Problems 314	
References 321	
chapter 7 Comparators 322	
7.1 Model of a Comparator 323	
7.2 Development of a CMOS Comparator 327	
7.3 Two-Stage Comparator 333	
7.4 Comparator with Hysteresis 349	
7.5 Auto Zero Techniques 357	
7.6 Summary 361	
Problems 361	
References 364	
chapter 8 Unbuffered CMOS Op Amps 365	
8.1 Op Amp Design Methodology 366	
8.2 Compensation of Op Amps 374	
8.3 Two-Stage Operational Amplifier Design 387	
8.4 Cascode Op Amps 403	
8.5 Simulation and Measurement of Op Amps 426	

8.6 Summary 446	
Problems 447	
References 455	
chapter 9 High-Performance CMOS Op Amps 456	
9.1 Op Amps Using an MOS Output Stage 457	
9.2 Op Amps Using MOS/BJT Output Stages 467	
9.3 High Speed/Frequency CMOS Op Amps 479	
9.4 Low-Noise Op Amps 487	
9.5 Chopper-Stabilized Op Amps 490	
9.6 Micropower Op Amps 497	
9.7 Dynamic Op Amp Circuits 504	
9.8 Summary 512	
Problems 513	
References 518	
chapter 10 CMOS Digital-Analog and Analog-Digital Converters 520	
10.1 Introduction and Characterization of Digital-Analog Converters 521	
10.2 Voltage- and Charge-Scaling D/A Converters 529	
10.3 Serial D/A Converters 544	
10.4 Introduction and Characterization of Analog-to-Digital Converters 550	
10.5 Serial A/D Converters 555	
10.6 Medium-Speed A/D Converters 560	
10.7 High Speed and High Performance A/D Converters 570	
10.8 Summary 585	
Problems 585	
References 587	
chapter 11 CMOS Analog Circuits and Systems 589	
11.1 Reference Sources 590	
11.2 Analog Multipliers 599	
11.3 Wave shaping Circuits 608	
11.4 Oscillators and Waveform Generators 633	
11.5 Summary and Conclusion 653	
Problems 655	
References 659	
appendix A Circuit Analysis for Analog Circuit Design 662	
appendix B Calculator Program for Analyzing CMOS Circuits 676	
appendix C Time-Frequency Domain Relationships for a Second-Order System 685	
Index 695	