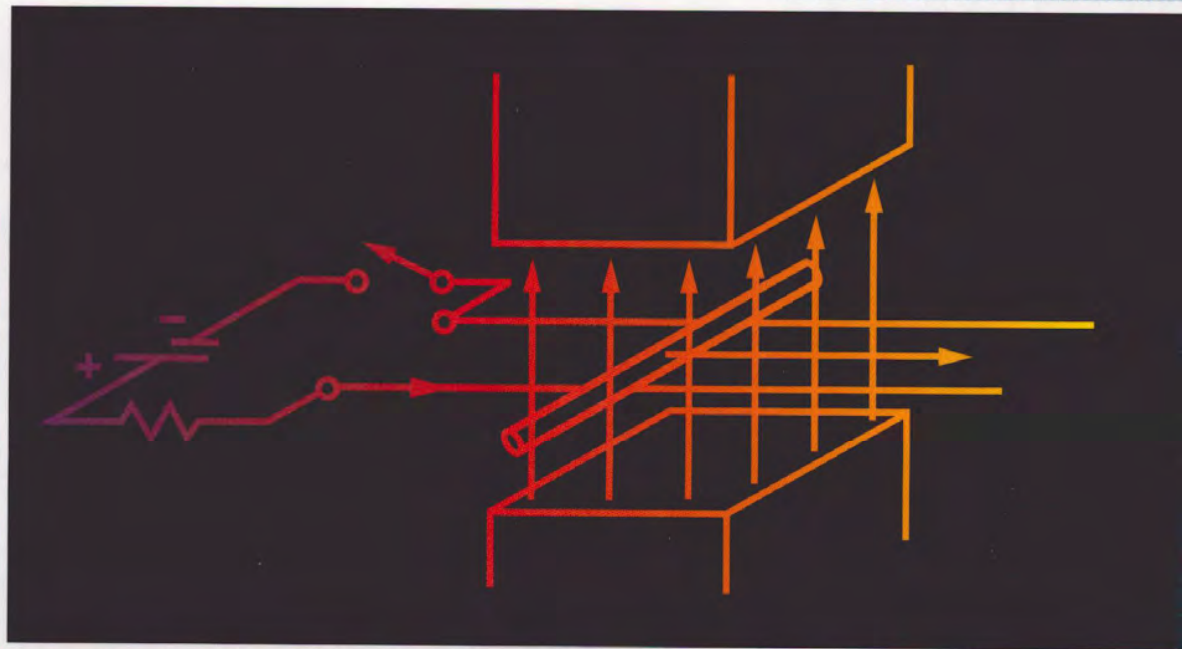


FOUNDATIONS OF
**ELECTRICAL
ENGINEERING**

S E C O N D  E D I T I O N



J. R. C O G D E L L

COGDELL



F O U N D A T I O N S O F
ELECTRICAL ENGINEERING

**SECOND
EDITION**



**PRENTICE
HALL**

FOUNDATIONS OF ELECTRICAL ENGINEERING

SECOND EDITION

J. R. COGDELL

A thorough revision of a popular text that is appropriate for introduction to electrical engineering courses for majors and non-majors. The author provides an in-depth, yet concise presentation of the important principles that form the basis of electrical engineering.

In this edition, the author has added real world applications from a variety of engineering disciplines, features that reinforce basic ideas and assist students in developing problem-solving skills, and engineering science and design material where appropriate. The clear organization and interesting features used in this text bring the understanding of circuits, electronics, systems, and electrical power engineering within the reach of all engineers.

Key Features

- More than **200 Examples** include problem statements, solutions, and What if? challenges that ask students to rework examples with a slight change.
- **Check Your Understanding** problems, which provide review and self-test for the student, follow most sections.
- Over **1,000** end-of-chapter **Problems** span a broad range of difficulty level.
- Recurrent fundamental concepts of electrical engineering are indicated throughout the text by **Idea icons**.
- **Objectives** are established at the beginning of each chapter. Material within the chapter that moves the student toward an objective is clearly indicated.

PRENTICE HALL
Upper Saddle River, NJ 07458

TSRN 0-13-092701-5



X00494MP8J

Foundations of Electrical Engineering, 2nd Edition
New

9"780130"927019"

Foundations of ELECTRICAL ENGINEERING

Second Edition

J . R . C O G D E L L

**Department of Electrical and Computer Engineering
University of Texas at Austin**



PRENTICE HALL

Upper Saddle River, New Jersey 07458

Library of Congress Cataloging-in Publication Data

Cogdell, J. R.

Foundation of electrical engineering / J. R. Cogdell. —2nd ed.

p. cm.

ISBN 0-13-092701-5

1. Electric engineering I. Title.

621.3—dc20

95—30313

CIP

1996

Acquisitions Editors: Alan Apt, Linda Ratts-Engelman

Production Editors: Joe Scordato/Rose Kernan

Developmental Editor: Sondra Chavez

Copy Editor: Peter Zurita

Text Designer: Delgado Design, Inc.

Cover Designer: Bruce Kenselaar

Manufacturing Buyer: Donna Sullivan

Editorial Assistant: Kathryn Cassino

Art Director: Amy Rosen

Creative Director: Paula Maylahn



© 1996, 1990 by Prentice Hall, Inc.

A Simon & Schuster/A Viacom Company

Upper Saddle River, New Jersey 07458

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission of the publisher.

Printed in the United States of America

10 9 8 7 6 5 4 3

ISBN 0-13-092701-5

Prentice Hall International (UK) Limited, *London*

Prentice Hall of Australia Pty. Limited, *Sydney*

Prentice Hall Canada Inc., *Toronto*

Prentice Hall Hispanoamericana, S.A., *Mexico*

Prentice Hall of India Private, Limited, *New Delhi*

Prentice Hall of Japan Inc., *Tokyo*

Simon & Schuster Asia Pte. Ltd, *Singapore*

Editora Prentice Hall do Brasil, Ltda., *Rio de Janeiro*

Brief Contents

PART 1 CIRCUITS

- 1 Basic Circuit Theory
- 2 The Analysis of DC Circuits
- 3 The Dynamics of Circuits
- 4 The Analysis of AC Circuits
- 5 Power in AC Circuits
- 6 Electric Power Systems

PART 2 ELECTRONICS

- 7 Semiconductor Devices and Circuits
- 8 Digital Electronics
- 9 Analog Electronics

PART 3 SYSTEMS

- 10 Instrumentation Systems
- 11 Communication Systems
- 12 Linear Systems

PART 4 MOTORS

- 13 The Physical Basis of Electromechanics
- 14 Magnetic Structures and Electrical Transformers
- 15 The Synchronous Machine
- 16 Induction Motors
- 17 Direct-Current Motors
- 18 Power Electronic Systems

Contents

Preface, XIII

PART 1 ■ CIRCUITS, 1

Chapter 1 Basic Circuit Theory, 2

Learning Objectives, 3

- 1.1 Introduction to Electrical Engineering, 4
Place of Electrical Engineering in Modern Technology, 4
- 1.2 Physical Basis of Circuit Theory, 5
Energy and Charge, 5
What Is Circuit Theory? 6
- 1.3 Current and Kirchhoff's Current Law, 7
Definition of Current, 7
Kirchhoff's Current Law, 10
Check Your Understanding, 12
- 1.4 Voltage and Kirchhoff's Voltage Law, 12
Definition of Voltage, 12
Kirchhoff's Voltage Law (KVL), 14
Check Your Understanding, 19
- 1.5 Energy Flow in Electrical Circuits, 19
Voltage, Current, and Power, 19
Check Your Understanding, 23
- 1.6 Circuit Elements: Resistances and Sources, 23
Resistances and Switches, 23
Voltage and Current Sources, 26
Analysis of DC Circuits, 28
Check Your Understanding, 33
- 1.7 Series and Parallel Resistances: Voltage and Current Dividers, 33

- Series Resistances and Voltage Dividers, 33
- Parallel Resistances and Current Dividers, 35
- Check Your Understanding, 40

Chapter Summary, 41

Problems, 42

Answers to Odd-Numbered Problems, 53

Chapter 2 The Analysis of DC Circuits, 54

Learning Objectives, 55

- 2.1 Superposition, 56
Superposition Illustrated, 56
Principle of Superposition, 57
Check Your Understanding, 61
- 2.2 Thévenin's and Norton's Equivalent Circuits, 61
Example to Justify the Concept, 61
Thévenin's Equivalent Circuit, 64
Impedance Level, 71
Source Transformations, 72
Check Your Understanding, 73
- 2.3 Node-Voltage Analysis, 74
Basic Idea, 74
Node-Voltage Technique, 76
Some Refinements, 78
Critique, 81
Check Your Understanding, 82

- 2.4 Loop-Current Analysis, **83**
 - Simple Method of Loop-Current Analysis, **83**
 - Some Extensions and Fine Points, **86**
 - Summary of Methods of Circuit Analysis, **90**
 - Check Your Understanding, **91**

Chapter Summary, **91**

Problems, **92**

Answers to Odd-Numbered Problems, **101**

Chapter 3 The Dynamics of Circuits, **102**

Learning Objectives, **103**

- 3.1 Theory of Inductors and Capacitors, **104**
 - Time and Energy, **104**
 - Inductor Basics, **104**
 - Capacitor Basics, **109**
 - Check Your Understanding, **114**
- 3.2 First-Order Transient Response of *RL* and *RC* Circuits, **114**
 - Classical Differential Equation Solution, **115**
 - A Simpler Method, **117**
 - RC* Circuits, **121**
- 3.3 Advanced Techniques, **122**
 - Circuits with Multiple Resistors, **122**
 - Initial and Final Values, **123**
 - Pulse Problem, **128**
 - Higher-Order Transients, **130**
 - An *RLC* Circuit, **133**
 - Check Your Understanding, **135**

Chapter Summary, **136**

Problems, **137**

Answers to Odd-Numbered Problems, **145**

Chapter 4 The Analysis of AC Circuits, **146**

Learning Objectives, **147**

- 4.1 Introduction to Alternating Current (AC), **148**
 - Importance of AC, **148**
 - Sinusoids, **148**
 - AC Circuit Problem, **152**
 - Check Your Understanding, **153**
- 4.2 Representing Sinusoids with Phasors, **153**
 - Sinusoids and Linear Systems, **153**

Mathematics of the Complex Plane, **154**

Phasor Idea, **161**

Back to the Circuit Problem, **163**

Check Your Understanding, **169**

- 4.3 Impedance: Representing the Circuit in the Frequency Domain, **170**
 - The Final Shortcut, **170**
- 4.4 Phasor Diagrams for *RL*, *RC*, and *RLC* Circuits, **175**
 - RL* Circuits, **176**
 - RC* Circuits, **180**
 - RLC* Circuits, **183**
 - Check Your Understanding, **186**

Chapter Summary, **186**

Problems, **188**

Answers to Odd-Numbered Problems, **196**

Chapter 5 Power in AC Circuits, **198**

Learning Objectives, **199**

- 5.1 AC Power and Energy Storage: The Time-Domain Picture, **200**
 - Importance of Power and Energy, **200**
 - Average Values of Electrical Signals, **200**
 - Effective or Root-Mean-Square (RMS) Value, **203**
 - Power and Energy Relations for *R*, *L*, and *C*, **207**
 - General Case for Power in an AC Circuit, **211**
 - Check Your Understanding, **215**
- 5.2 Power and Energy in the Frequency Domain, **216**
 - Real and Reactive Power from Phasors, **216**
 - Complex Power, **219**
 - Reactive Power in Power Systems, **223**
 - Reactive Power in Electronics, **225**
 - Check Your Understanding, **229**
- 5.3 Transformers, **229**
 - Transformer Principles, **229**
 - Transformer Applications in AC Power Systems, **236**
 - Residential AC Power, **240**

Electrical Safety, 242

Check Your Understanding, 246

Chapter Summary, 246

Problems, 248

Answers to Odd-Numbered Problems, 256

Chapter 6 Electric Power Systems, 258

Learning Objectives, 259

6.1 Three-Phase Power, 260

Importance of Electric Power Systems, 260

Introduction to Three-Phase Power Systems, 260

Three-Phase Power Sources, 262

Three-Phase Loads, 267

Per-Phase Equivalent Circuits, 275

Check Your Understanding, 277

6.2 Power Distribution Systems, 277

Three-Phase Transformers, 278

Per-Unit Calculations, 281

Transmission Properties, 283

Check Your Understanding, 286

6.3 Introduction to Electric Motors, 287

Terminology, 287

Motor Characterization in Steady-State Operation, 288

The Motor with a Load, 289

Dynamic Operation, 291

Three-Phase Induction Motor Nameplate Interpretation, 292

Single-Phase Induction Motor, 298

Check Your Understanding, 299

Chapter Summary, 299

Problems, 300

Answers to Odd-Numbered Problems, 310

PART 2 ■ ELECTRONICS, 311

Chapter 7 Semiconductor Devices and Circuits, 312

Learning Objectives, 313

7.1 Rectifiers and Power Supplies, 314

Introduction to Electronics, 314

Ideal Diode, 315

Rectifier Circuits, 317

Rectifier with Filter Capacitor, 322

Check Your Understanding, 325

7.2 The *pn*-Junction Diode, 326

Semiconductor Processes and the *pn* Junction, 326

Physical Properties of Real Diodes, 332

Check Your Understanding, 335

7.3 Bipolar-Junction-Transistor (BJT)

Operation, 335

Importance of the Transistor, 335

BJT Characteristics, 337

BJT Output Characteristics, 338

Transistor Amplifier-Switch Circuit

Analysis, 340

Transistor Applications, 345

Small-Signal Amplifiers, 346

Check Your Understanding, 352

7.4 Field-Effect Transistors, 352

Junction Field-Effect Transistors, 352

JFET Applications, 356

Metal-Oxide Semiconductor Field-Effect Transistors (MOSFETs), 360

Check Your Understanding, 363

Chapter Summary, 363

Problems, 364

Answers to Odd-Numbered Problems, 379

Chapter 8 Digital Electronics, 380

Learning Objectives, 381

8.1 Digital Information, 382

What Is a Digital Signal? 382

Digital Representation of Information, 384

Check Your Understanding, 386

8.2 The Electronics of Digital Signals, 387

NOT Circuit, 387

BJT Gates, 389

MOSFET Gates, 391

Check Your Understanding, 392

8.3 The Mathematics of Digital Electronics, 392
Need for a Mathematical Language, 392
Common Boolean Theorems, 393
Check Your Understanding, 396

8.4 Combinational Digital Systems, 396
Logic Symbols and Logic Families, 396
Realization of Logic Functions, 398
Binary Arithmetic, 399
Digital Arithmetic Circuits, 402
Karnaugh Maps, 404
Check Your Understanding, 407

8.5 Sequential Digital Systems, 407
Bistable Circuit, 407
Latches and Flip-Flops, 409
Flip-Flop Applications, 414
Check Your Understanding, 419

8.6 Computers, 419
Introduction, 419
Computer Architecture, 420

Chapter Summary, 423

Problems, 424

Answers to Odd-Numbered Problems, 434

Chapter 9 Analog Electronics, 438

Learning Objectives, 439

9.1 Frequency-Domain Representation of Signals, 440
Introduction, 440
Frequency-Domain Representation of Periodic Functions, 441
Spectra of Nonperiodic Signals, 447
Spectra of Random Signals, 454
Bandwidth and Information Rate, 458
Check Your Understanding, 460

9.2 Electrical Filters, 460
Filter Concepts, 460
Bode Plots, 465
Check Your Understanding, 473

9.3 Feedback Concepts, 474
A Feedback Amplifier, 474

System Model, 476

Benefits of Negative Feedback, 479

Check Your Understanding, 489

9.4 Operational-Amplifier Circuits, 489
Introduction, 489
Basic Op-Amp Amplifiers, 491
Linear Op-Amp Circuits, 496
Nonlinear Op-Amp Circuits, 502
Check Your Understanding, 505

Chapter Summary, 505

Problems, 506

Answers to Odd-Numbered Problems, 518

PART 3 ■ SYSTEMS, 521

Chapter 10 Instrumentation Systems, 522

Learning Objectives, 523

10.1 Introduction to Instrumentation Systems, 524
General Considerations, 524
Transducers, 525
Error Analysis, 530
Check Your Understanding, 533

10.2 Analog Signal Processing, 534
Instrumentation Amplifiers, 534
Analog Active Filters, 538
Cabling, Grounding, and Shielding Techniques, 546
Check Your Understanding, 548

10.3 Digital Signal Processing, 548
Analog-to-Digital Conversion, 548
Sampling, 552
Digital-to-Analog Conversion, 557
Check Your Understanding, 560

Chapter Summary, 560

Problems, 561

Answers to Odd-Numbered Problems, 566

Chapter 11 Communication Systems, 568

Learning Objectives, 569

11.1 Radio Principles, 570

General Principles of Nonlinear Devices in the Frequency Domain, 570	
Modulation and Demodulation, 572	
Radio Receivers, 578	
Noise in Receivers, 586	
Check Your Understanding, 590	
11.2 Electromagnetic Waves, 591	
Guided Electromagnetic Waves, 592	
Free Electromagnetic Waves, 594	
Antennas, 597	
Check Your Understanding, 603	
11.3 Examples of Communication Systems, 604	
FM Broadcast Station, 604	
Speed-Measuring Radar, 605	
Chapter Summary, 607	
Problems, 608	
Answers to Odd-Numbered Problems, 610	
Chapter 12 Linear Systems, 612	
Learning Objectives, 613	
Introduction to Linear Systems, 614	
12.1 Complex Frequency, 614	
Check Your Understanding, 618	
12.2 Impedance and the Transient Behavior of Linear Systems, 619	
Generalized Impedance, 619	
Transient Analysis, 620	
Frequency Response, 628	
Check Your Understanding, 629	
12.3 Transient Response of RLC Circuits, 630	
Types of Natural Responses in RLC Circuits, 630	
RLC Circuit Transient Behavior, 632	
Check Your Understanding, 636	
12.4 System Analysis, 636	
System Functions, 636	
Dynamic Stability of Feedback Systems, 638	
Chapter Summary, 642	
Problems, 643	
Answers to Odd-Numbered Problems, 649	

PART 4 ■ MOTORS, 651

Chapter 13 The Physical Basis of Electromechanics, 652

Learning Objectives, 653

Introduction to Electromechanics, 654

13.1 Electric Forces and Electric Fields, 654

Forces between Charges, 654

Electric Fields, 655

Check Your Understanding, 658

13.2 Magnetic Forces and Magnetic Fields, 658

Current and Magnetic Forces, 658

Direction of the Magnetic Field, 661

Magnetic Effects in Matter, 662

Magnetic Flux (Φ) and Magnetic-Flux

Linkage (λ), 666

Check Your Understanding, 667

13.3 Dynamic Magnetic Systems, 667

Induced Voltage, 667

Stored Energy in a Magnetic System, 671

Conductors Moving in Magnetic Flux, 673

Electromechanical Energy Conversion, 675

Check Your Understanding, 678

Chapter Summary, 678

Problems, 680

Answers to Odd-Numbered Problems, 686

Chapter 14 Magnetic Structures and Electrical Transformers, 688

Learning Objectives, 689

14.1 Analysis of Magnetic Structures, 690

Introduction to Magnetic Structures, 690

Toroidal Ring, 691

Principles of Analysis of Magnetic Structures, 693

Check Your Understanding, 695

14.2 Electrical Transformers, 696

Introduction to Transformers, 696

Analysis of a Transformer as a Magnetic Structure, 697

Transformer Equivalent Circuits, 700

Transformer Open-Circuit (OC)/Short-Circuit (SC) Test, **702**

Why Voltage and Apparent Power (kVA)

Rating Are on the Nameplate, **707**

Models of Three-Phase Transformers, **708**

Check Your Understanding, **711**

14.3 Forces in Magnetic Systems, 711

Magnetic-Pole Approach, **711**

Analysis from Current-Flux Interaction, **713**

Analysis from Energy Considerations, **713**

Coenergy and Magnetic Force, **718**

Circuit Approach, **720**

Check Your Understanding, **721**

Chapter Summary, **721**

Problems, **722**

Answers to Odd-Numbered Problems, **740**

Chapter 15 The Synchronous Machine, 744

Learning Objectives, **745**

Introduction to Motor/Generators, **746**

Conditions for Motor/Generator Action, **747**

15.1 Flux and Torque in Cylindrical Magnetic Structures, 748

Analysis of Cylindrical Magnetic Structures, **748**

Torque Development between Rotor and Stator Fluxes, **751**

Check Your Understanding, **754**

15.2 Rotating Magnetic Flux for AC Motors, 754

Two-Phase Rotating Flux, **754**

Three-Phase Rotating Flux, **757**

Single-Phase Flux Expressed as a Rotating Flux, **758**

Check Your Understanding, **760**

15.3 Synchronous Generator Principles and Characteristics, 761

Synchronous Generator Construction and Equivalent Circuit, **761**

Generator Operation in Stand-Alone Power Systems, **764**

Power Angles, **766**

Synchronous Generator Operation in a Large Power System, **767**

Check Your Understanding, **771**

15.4 Characteristics of the Synchronous Motor, 772

Generator and Motor Comparison, **772**

Salient-Pole Motors, **776**

Check Your Understanding, **779**

Chapter Summary, **779**

Problems, **780**

Answers to Odd-Numbered Problems, **792**

Chapter 16 Induction Motors, 794

Learning Objectives, **795**

Introduction to Induction Motors, **796**

16.1 Induction-Motor Principles, 796

Induction Principles, **796**

Developed Torque, $T_{dev}(\omega_s)$, **799**

Three-Phase Induction-Motor

Characteristics, **800**

Check Your Understanding, **804**

16.2 Equivalent Circuit for a Three-Phase Induction Motors, 805

Physical Basis for Equivalent Circuit, **805**

Applications of Equivalent Circuit, **809**

Dynamic Response of Induction Motors, **816**

Motor-Size Choice for Fluctuating Load Torque, **822**

Check Your Understanding, **825**

16.3 Single Phase Induction Motors, 826

Check Your Understanding, **831**

Chapter Summary, **832**

Problems, **833**

Answers to Odd-Numbered Problems, **843**

Chapter 17 Direct-Current Motors, 844

Learning Objectives, **845**

17.1 Principles of DC Machines, 846

Stator Magnetic Structure, **846**

Rotor Construction, **848**

Circuit Model, **850**

Power Flow in DC Machines, **851**

- Check Your Understanding, **855**
- 17.2** Characteristics of DC Motors, **856**
 Shunt-Connected Field, **856**
 Series-Connected Field, **861**
 Universal (AC/DC) Motors, **863**
 Check Your Understanding, **864**
- 17.3** Dynamic Response of DC Motors, **865**
 Current-Driven Motor Dynamics, **866**
 Voltage-Driven Motor Dynamics, **868**
 Check Your Understanding, **870**
- Chapter Summary, **871**
 Problems, **871**
 Answers to Odd-Numbered Problems, **880**

Chapter 18 Power Electronic Systems, 882

Learning Objectives, 883

- 18.1** Introduction to Power Electronics, **884**
 Semiconductor Switches, **884**
 Common Application of Power Electronics, **891**

Check Your Understanding, 896

- 18.2** DC Motor Controllers, **897**
 Introduction to Motor Controllers, **897**
 DC Motor Model, **899**
 Single-Phase Uncontrolled Rectifier Analysis, **900**
 Controlled Rectifier Operation: Constant-Speed Analysis, **904**
 Motor Performance with Constant Firing Angle, **911**
 Check Your Understanding, **913**
- 18.3** AC Motor Controllers, **914**
 DC-Link Variable-Frequency Controllers, **917**
 Check Your Understanding, **922**

Chapter Summary, 922

Problems, 923

- Answers to Odd-Numbered Problems, **934**
 Index, **935**

1. To explain well the fundamental ideas of electrical engineering.
2. To emphasize the unity of the subject by frequent reminders of those basic ideas.
3. To bring understanding of circuits, electronics, systems, and electrical power engineering within the reach of all engineers.

My equal emphasis on electrical power engineering meets, I predict, an emerging need of our time. In the eyes of EE students, the technical challenge, professional opportunities, and personal enjoyment of electronics have totally eclipsed interest in electric power engineering. To most students, comparing power and electronics is like comparing a draft horse with a racing thoroughbred, with the result that many electrical engineering students avoid taking a single elective course in power. Thus, electric motors, like illumination engineering, must fall to the engineer who needs the information, such as the mechanical engineer who needs to select a motor to drive a pump. This book anticipates the need of all engineers to have more than superficial knowledge of electric power, motors, in particular.

IMPROVEMENTS IN THE SECOND EDITION

While sharing in the goals of the first edition, this second edition differs in many ways. The entire text has been revised and refined, a new chapter has been added, and material has been rearranged to improve the logic and flow. The presentation has been im-

$$L_{eq} = L_1 \parallel L_2 = \frac{1}{1/L_1 + 1/L_2} \text{ (parallel inductors)} \quad (3.9)$$

Capacitor Basics

Physical capacitors. Electric (electrostatic) forces arise from interactions between separated charges, and the associated energy is called electric energy. To store electric energy, we must separate charges, as in Fig. 3.9.

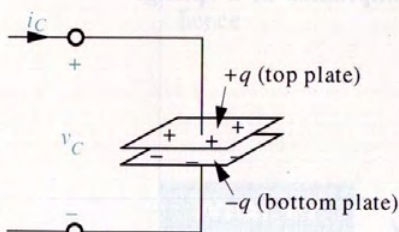


Figure 3.9 Structure having capacitance.

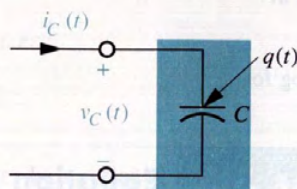


Figure 3.10 Circuit symbol for capacitance.

OBJECTIVE 2

To understand the properties of capacitors and to be able to find the capacitor voltage from the capacitor current and vice versa

Circuit-theory definition of a capacitor. Figure 3.10 shows the circuit symbol for a capacitance. Capacitance is defined as the constant relating charge and voltage in a structure that supports a charge separation. If q is the charge on the + side of the capacitor and the voltage is v_C , as shown in Fig. 3.9, the capacitance, C , is defined as

$$q = Cv_C \quad (3.10)$$

Chapter 13 discusses the physics of capacitance. For every charge arriving at the + side of the capacitor, a charge of like sign will depart from the - side and the structure as a whole will remain charge-neutral. Thus, KCL will be obeyed because charge flowing into the + terminal side is matched by charge flowing out of the - terminal, as for a resistor. If current is positive into the + terminal, positive charge will accumulate there and will be increasing in proportion to the current. From the definition of current, we can relate the charge in Eq. (3.10) and current as follows:

$$i_C = \frac{dq(t)}{dt} \quad (3.11)$$

where $q(t)$ is the charge in the + side of the capacitor. Thus, we may define the relationship between current and voltage for a capacitor as

$$i_C = \frac{d}{dt} Cv_C(t) = C \frac{dv_{C(t)}}{dt} \quad (3.12)$$

where the last form of Eq. (3.12) is valid if the capacitance is constant. Note that we have used a load set in Fig. 3.10 for the voltage and current variables.

Units of capacitance. The unit of capacitance is the coulomb/volt, but to honor Michael Faraday (1791–1867), we use the name *farad* (F). Realistic capacitor values come small and usually are specified in microfarads (10^{-6} F, or μF), nanofarads (10^{-9} F, or nF), or picofarads (10^{-12} F, or pF). When a capacitor is constructed from parallel

farad,
microfarad,
nanofarad,
picofarad

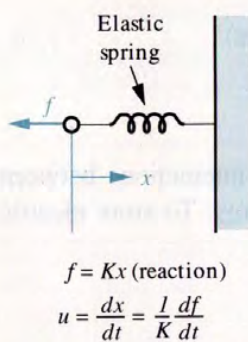


Figure 3.11
Mechanical analog for capacitance.

plates, as in Fig. 3.9, the capacitance depends on the area, separation, and material (if any) between the plates.

Mechanical analog of capacitance. The mechanical analog of a capacitor is a spring, as shown in Fig. 3.11. The analog of velocity is current and thus displacement of the spring is analogous to charge. The voltage across a capacitor is analogous to the force produced by the spring. Comparison of the second equation in Fig. 3.11 with Eq. (3.12) shows that capacitance corresponds to the inverse of the stiffness constant, K , and thus capacitance is analogous to the compliance of a spring.

EXAMPLE 3.3 Equation of RC circuit

Derive the equation for the current in Fig. 3.12(a). Assume $v_C(0) = 0$.

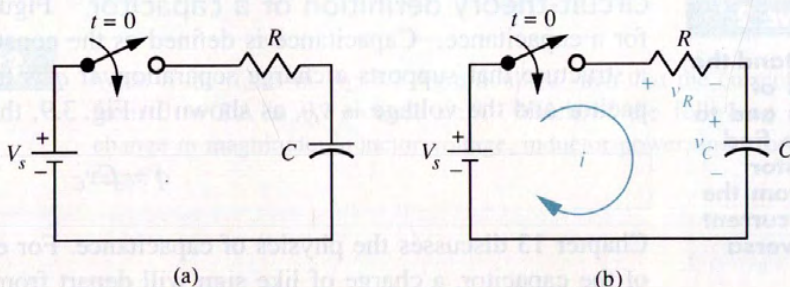


Figure 3.12 (a) Closing the switch will cause a momentary current. (b) The same circuit with variables defined.

SOLUTION:

Figure 3.12(b) defines the capacitor and resistor voltages in a load-set convention. With the switch closed, KVL is

$$-V_s + v_R(t) + v_C(t) = 0 \quad (3.13)$$

We may express both voltages in terms of the current if we differentiate Eq. (3.13):

$$0 + \frac{d}{dt} Ri(t) + \frac{dv_C(t)}{dt} = R \frac{di(t)}{dt} + \frac{i(t)}{C} = 0 \quad (3.14)$$

The last form in Eq. (3.14) is readily manipulated to the form

$$\frac{di}{i} = -\frac{1}{RC} dt \Rightarrow \ln i = -\frac{t}{RC} + \ln A \Rightarrow i(t) = Ae^{-t/RC} \quad (3.15)$$

where A is a constant. The current will charge the capacitor until the capacitor voltage is equal to the battery voltage. Equation (3.16) equates the final charge on C to the integral of the current.

$$q - q(0) = CV_s = \int_0^{\infty} i(t) dt = \frac{Ae^{-t/RC}}{-1/RC} \bigg|_0^{\infty} = A(RC) \quad (3.16)$$

Because $v_C(0) = 0$, $q(0) = 0$, and

$$A = \frac{V_s}{R} \quad (3.17)$$

hence

$$i(t) = \frac{V_s}{R} e^{-t/RC} \quad (3.18)$$

WHAT IF?

What if the switch is opened after being closed a long time? What would happen to the capacitor voltage?⁴

Integral i - v equation. Equation (3.12) is useful in determining the current through a capacitor, given the voltage as a function of time. If we know the current and wish to determine the voltage, we must integrate. Let us consider that we know the capacitor voltage at some time, say, $t = 0$, and wish to determine the voltage at a later time, t . We can integrate Eq. (3.12) from 0 to t , with the result

$$v_C(t) = v_C(0) + \frac{1}{C} \int_0^t i_C(t') dt' \quad (3.19)$$

We have used t' as the dummy variable of the integration process because t is one limit of the integral.

EXAMPLE 3.4 Capacitor discharge and charge

As an example of the use of Eq. (3.19), consider a capacitor with current, as shown in Fig. 3.13.

Here we know the voltage at the beginning time, $v_C(0) = -2$ V, and the current through the capacitor. We wish to compute the voltage for all $t > 0$. We will use Eq. (3.19), noting that we must divide the integration into several regions due to the piecewise nature of the current function. During interval I, $0 < t < 1$ ms, the current is zero; hence, the voltage does not change. During interval II, the slope of the current is 0.1 A/1 ms = 100 A/s; hence, the current is

⁴ No current could flow after the switch opened, and according to Eq. (3.12), the voltage would remain constant. A real capacitor would discharge over time due to leakage current.

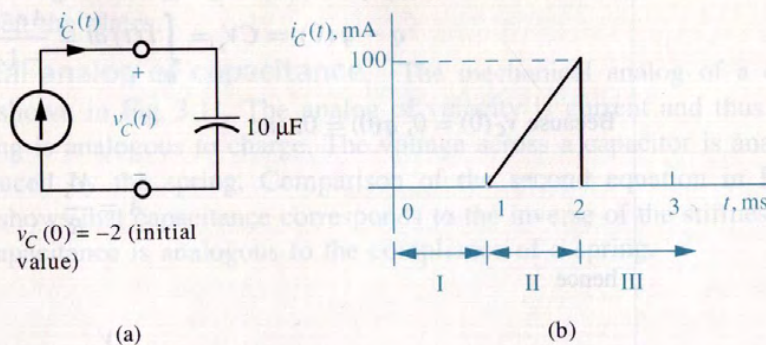


Figure 3.13 (a) The capacitor has an initial voltage. (b) Current into the capacitor for positive time.

$$i_C(t) = 100(t - 1 \text{ ms}) \text{ A}, \quad 1 \text{ ms} < t < 2 \text{ ms} \quad (3.20)$$

Thus, during interval II, the voltage will be

$$\begin{aligned} v_C(t) &= -2.0 + \frac{1}{10 \mu\text{F}} \int_{1 \text{ ms}}^t 100(t' - 1 \text{ ms}) dt' \Big|_{\text{II}: 1 < t < 2 \text{ ms}} \\ &= -2.0 + \frac{10^{-5} \times 100 (t - 1 \text{ ms})^2}{2} \text{ V} \end{aligned} \quad (3.21)$$

which indicates a parabolic increase, as shown in Fig. 3.14. The final value at $t = 2 \text{ ms}$ is $+3 \text{ V}$, which is easily checked from the area under the current curve:

$$\Delta v_C = \frac{\Delta q}{C} = \frac{\text{area under current curve}}{C} = \frac{\frac{1}{2} \times 1 \text{ ms} \times 100 \text{ mA}}{10 \mu\text{F}} = +5 \text{ V} \quad (3.22)$$

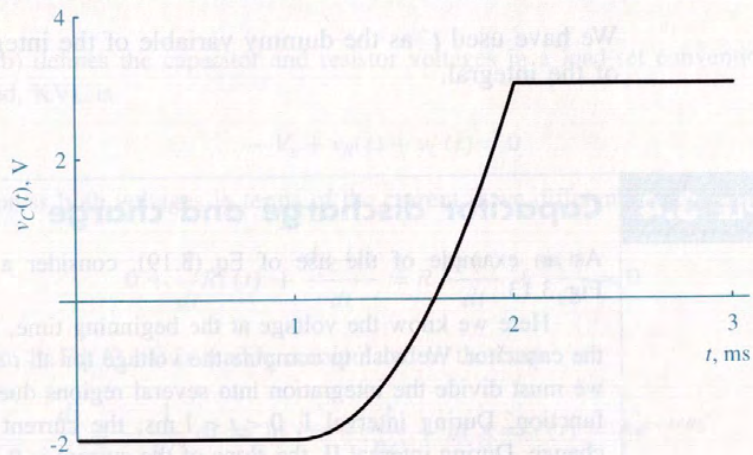


Figure 3.14 Capacitor voltage for positive time.

After the current pulse, the capacitor voltage remains constant because the current is zero. This

constant voltage would hold for an ideal capacitor; a physical capacitor would discharge eventually due to leakage current.

WHAT IF?

What if the current were constant at 100 mA for $1 \text{ ms} < t < 2 \text{ ms}$? What then would be the final value?⁵

Mechanical analogy. The process of integrating current through a capacitor to determine voltage is analogous to integrating velocity to determine change in force in a spring problem. The only difference is that the value of the capacitance scales the integral of the current, whereas the scale factor depends on K , the spring constant, in the mechanical analog.

Stored energy in a capacitor. The charge separation in a capacitor stores electric energy. This energy is analogous to potential energy stored in a stressed spring. We may derive the stored electric energy in a capacitor by integrating the power into the capacitor,

$$W_e = \int p_C dt = \int v_C \times C \frac{dv_C}{dt} dt = \int d\left(\frac{1}{2} C v_C^2\right) = \frac{1}{2} C v_C^2 = \frac{1}{2} \frac{q^2}{C} \quad (3.23)$$


where p_C is the power into the capacitor and W_e is the stored electric energy in the capacitor. The constant of integration must be zero because the uncharged capacitor stores no energy. We see from Eq. (3.23) that the stored energy depends uniquely on the voltage, or the charge, and the capacitance. For example, if we take a $10\text{-}\mu\text{F}$ capacitor and connect it briefly to a 12.6-V battery, the capacitor will receive $0.5 \times 10^{-5} (12.6)^2 = 7.94 \times 10^{-4} \text{ J}$ from the battery. Although this is not much energy, it would take only about $1 \mu\text{s}$ to charge the capacitor. Hence, the rate of energy flow would be rather high, about 800 W .



Equivalent Circuits

Figure 3.15

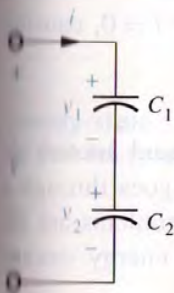Capacitors in series add like resistors in parallel: $C_{eq} = C_1 \parallel C_2$.



Capacitors in series and parallel. Figure 3.15 shows two capacitors in series. KVL yields

$$v(t) = v_1 + v_2 = \frac{1}{C_1} \int_0^t i dt + \frac{1}{C_2} \int_0^t i dt = \frac{1}{C_{eq}} \int_0^t i dt \quad (3.24)$$

where

$$C_{eq} = C_1 \parallel C_2 = \frac{1}{1/C_1 + 1/C_2} \quad (\text{series capacitors})$$

Thus, capacitors connected in series combine numerically like resistors in parallel. Similarly, we can easily show that capacitors in parallel add like resistors in series, that is,

$$C_{eq} = C_1 + C_2 \quad (\text{parallel capacitors}) \quad (3.25)$$

Mechanical analog for resistance. A mechanical analog for a resistance is frictional loss of a special type. Voltage is analogous to force, and current analogous to ve-

⁵+8 V.

TABLE 3.1 Summary of Mechanical and Electrical Analogs

Mechanical	Electrical
Force	Voltage
Velocity	Current
Displacement	Charge
Mass	Inductance
Spring compliance	Capacitance
Shock absorber	Resistance

locity. Voltage/current, or resistance, would thus imply a force that is proportional to velocity. We experience such a force when we try to move underwater. A common mechanical component having this property would be an automotive shock absorber. Table 3.1 summarizes the analogies between mechanical and electrical quantities.

**Check Your Understanding**

1. An inductor has a stored energy of 5 J and an inductance of 0.1 H. What is the current through the inductor?
2. If an ideal 10-V battery were connected for 1 s to an ideal 1-H inductor, how much energy would be given to the inductor?
3. A capacitor has a stored energy of 500 μJ and a capacitance of 0.15 μF . What is the voltage across this capacitor?
4. What is the mechanical analog of an inductor?

Answers. (1) 10 A; (2) 50.0 J; (3) 81.6 V; (4) mass.

3.2 FIRST-ORDER TRANSIENT RESPONSE OF RL AND RC CIRCUITS**transients,
first-order transient**

First-order transients. In the major part of this chapter, we show how to analyze an important class of circuit problems. Typical situations are shown in Fig. 3.16. These circuits are characterized by having the following:

- A single energy storage element, one capacitor or inductor
- Loss, represented by one or more resistors
- DC sources
- A switch⁶ that either opens or closes at a known time, usually $t = 0$, causing a sudden change in the circuit
- Only linear components.

In all cases, the circuit will have one dc state before the switch action and another dc state long after the switch action. Consequently, the state of the circuit goes through a transition. Because this transition lasts for a brief period of time, these problems are often called *transient* problems. We consider primarily circuits with one energy storage element, which lead to *first-order transients*.

⁶The pulse in Fig. 3.16(c) can be considered a voltage switched ON, then OFF.

mately 10–12 pulses/second and relays counted the pulses at the exchange to route the call. The ring signal was about 90 to 100 V ac at approximately 20 Hz.

The modern system used a tone system to transmit switching information and semiconductor switching computers have replaced the relays. The “ring” signal is commonly a tone that activates an audible device in the telephone receiver.

The local exchange switches up to 10^4 lines with the signal at the base band with a 4-kHz bandwidth. Between exchanges, the voice information is modulated with signal sideband plus carrier into groups of 12 adjacent channels between 60 and 108 kHz. These groups, 12 channels, are then placed into a supergroup of 60 channels between 312 and 552 kHz, and finally 10 supergroups, 600 channels, are placed into a master-group between 564 and 3084 kHz. For long distance, the voice channels are modulated to yet higher frequency for transmission by coaxial cable, line-of-sight microwave, or satellite link. Currently digital systems using optical fibers are replacing traditional analog systems.

Noise in Receivers



Digital Information

noise, interference

Importance of noise. When we spoke of op amps in Chapter 9, we asserted that gain is cheap. With radio receivers, gain is not as cheap as with op amps, but we can still achieve as high a gain as we wish by adding more stages of amplification. We might suppose, therefore, that we can successfully detect any input RF signal, no matter how weak, simply by having adequate gain in the receiver. This is not true, however, because the sensitivity of a radio receiver is limited by random noise. *Noise*, by definition, is any undesired signal in the system, whether natural or man-made. Man-made noise is called *interference*; Chapter 10 showed techniques to reduce its effects.

blackbody radiation, shot noise, flicker noise

Sources of natural noise. Natural noise in communication systems comes from two sources. Some noise comes into the receiver from the antenna; for example, in an AM receiver, we can hear a sporadic crackling noise from lightning during storms. Other sources of noise that enter the system through the antenna are atmospheric gases (thermal noise) and extraterrestrial objects such as the sun and our galaxy (cosmic noise).

The second source of noise is the receiver itself. Just as any body radiates *blackbody radiation* due to the thermal motion of its atomic constituents, so also resistors radiate their own type of thermal noise into the circuits of which they are a part. We investigate resistor noise in what follows. Transistors add, in addition to thermal noise, *shot noise* due to the discrete charges that carry the current across the *pn* junctions, and *flicker* or *1/f* noise, due to slow changes in device properties from aging, temperature, and other physical changes.



Equivalent Circuits



The Frequency Domain

white noise

Thermal noise. The thermal radiation of resistors plays an important role in the description of noise because resistors provide a simple calibration for noise signals. Figure 11.16(a) shows a resistor, R , and indicates the noise voltage generated by the thermal motion of the carriers in the resistor. The Thévenin equivalent circuit in Fig. 11.16(b) separates the noise voltage from the resistance, which here is noise-free. The power spectrum of the noise voltage in volts²/hertz is shown in Fig. 11.16(c),

$$S_n(f) = 4kTR \text{ V}^2/\text{Hz} \quad (11.14)$$

with k = Boltzmann’s constant of 1.38×10^{-23} J/K. We note the following:

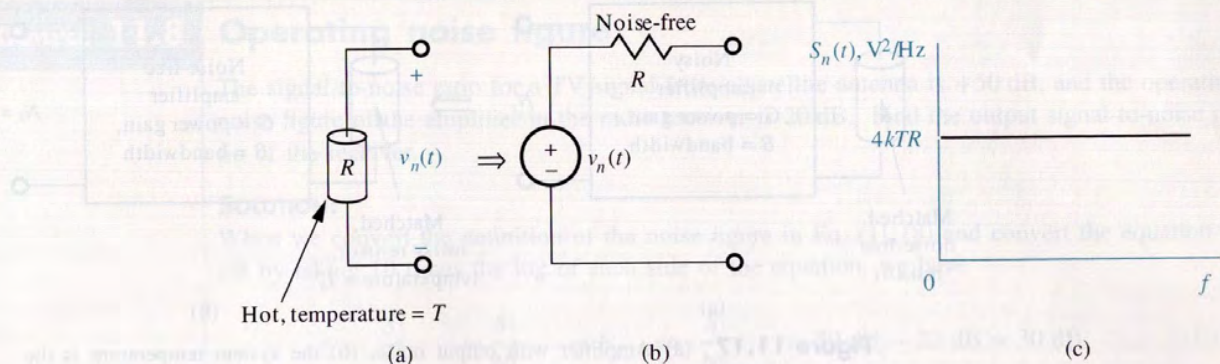


Figure 11.16 (a) A noisy resistor; (b) Thévenin equivalent circuit of a noisy resistor; (c) power spectrum of thermal noise.

- The noise spectrum is *white noise*, meaning that all frequencies are present equally, at least throughout the radio spectrum. Thus, a resistor produces a noise power that is proportional to the bandwidth of the circuit.
- The intensity of the power spectrum is proportional to the temperature of the resistor. For sensitive amplifiers, we may measure the noise of the system by comparing system noise to the noise from a resistor of known temperature.
- The intensity of the power spectrum is proportional to the resistance. For this reason, large values of resistance are avoided in sensitive electronic amplifiers. The *available power* out of a circuit is the maximum power that the circuit is capable of delivering into a matched load (see Chapter 2, page 69). The available power spectrum from the circuit in Fig. 11.16(b) is.

available power

$$S_{av}(f) = \frac{S_n(f)}{4R} = kT \text{ W/Hz} \quad (10.15)$$

where $S_{av}(f)$ is the available power spectrum in watts/hertz. Thus, the total power a noisy resistor will contribute to a matched circuit is

$$P = kTB \text{ W} \quad (11.16)$$

where B is the bandwidth in hertz. Equation (11.16) is useful in determining the signal-to-noise ratio in a communication circuit, once we have defined the noise figure and system temperature of an amplifier.

system temperature

System temperature. The noise originating in the resistors and semiconductors in a radio amplifier is generally broadband or white noise, at least over the bandwidth of the radio. Thus, we may represent the noise *as if* it originated in a resistor at the input of the radio. Figure 11.17(a) shows the true situation: An amplifier with a power gain of G and a bandwidth of B has internal noise sources that produce N_s watts of noise at its output. In Fig. 11.17(b) we show an equivalent amplifier, assumed to be noise-free, with the same noise at its output *attributed* to a noisy resistor at the input. The *system temperature* is defined as the temperature the resistor required in Fig. 11.17(b) to produce the same amount of output noise as in Fig. 11.17(a). Using Eq. (11.16), we can express

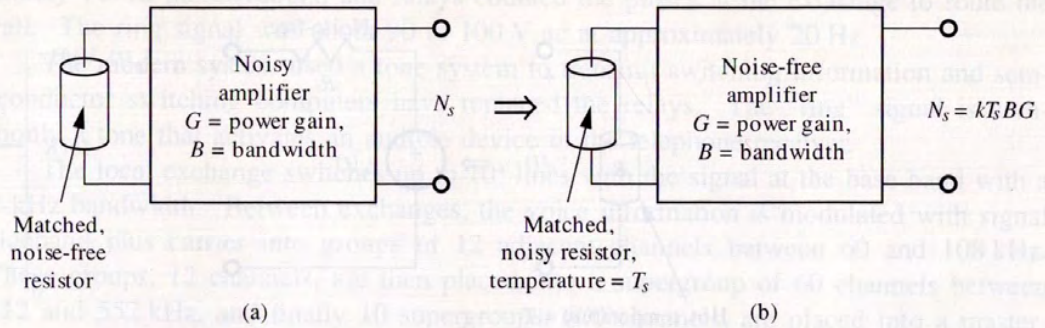


Figure 11.17 (a) Amplifier with output noise; (b) the system temperature is the temperature of the input resistor to give the same output noise.

the output noise as

$$N_s = kT_s GB \Rightarrow T_s = \frac{N_s}{kGB} \text{ K} \quad (11.17)$$

where T_s is the system temperature and N_s is the output noise produced by the amplifier. All the internally generated noise is *referred to the input* of the receiver and then expressed as a temperature. The system temperature describes the sensitivity of the amplifier; the lower the system temperature, the more sensitive the amplifier.

operating noise figure

Noise figure. The *operating noise figure* is defined as the input signal-to-noise ratio divided by the output signal-to-noise ratio. Figure 11.18 shows an amplifier with input signal and noise, S_{in} and N_{in} , and output signal and noise, S_{out} and N_{out} . The *operating noise figure* is defined to be

$$F = \frac{S_{in}/N_{in}}{S_{out}/N_{out}} = \frac{N_{out}}{N_{in}G} = \frac{N_{in}G + N_s}{N_{in}G} = 1 + \frac{N_s/G}{N_{in}} = 1 + \frac{T_s}{T_{in}} \quad (11.18)$$

where F is the operating noise figure of the amplifier and is often expressed in decibels: $F_{dB} = 10 \log F$ and T_{in} is the input noise expressed as a temperature. The first form on the right side of Eq. (11.18) is the definition of operating noise figure. The second form introduces the gain, $G = S_{out}/S_{in}$, and the third form breaks the output noise into two components, the amplified input noise and the internally generated noise. The last form shows that the noise figure depends on the internally generated noise, referred to the input of the amplifier, compared with the input noise. Thus, the operating noise figure depends in part on the input noise and not on the amplifier only. The operating noise figure is useful in performing signal-to-noise calculations in a communication system.

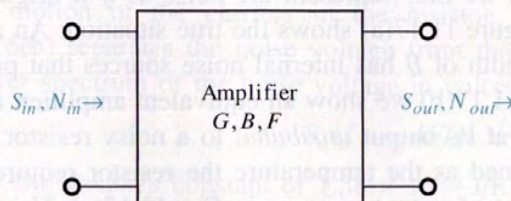


Figure 11.18 Amplifier with signal and noise at input and output.