

Microelectronic Circuits

FOURTH EDITION

Sedra/Smith

CD-ROM
Enclosed



Now with 600
Additional Problems
and a **FREE COPY** of
Electronics Workbench
Multisim® 2001
Textbook Edition
on CD!



MICROELECTRONIC CIRCUITS

The Oxford Series in Electrical and Computer Engineering

M.E. Van Valkenburg, *Senior Consulting Editor*

Adel S. Sedra, *Series Editor, Electrical Engineering*

Michael R. Lightner, *Series Editor, Computer Engineering*

ALLEN AND HOLBERG CMOS Analog Circuit Design

BOBROW Elementary Linear Circuit Analysis, 2nd Ed.

BOBROW Fundamentals of Electrical Engineering, 2nd Ed.

CAMPBELL The Science and Engineering of Microelectronic Fabrication

CHEN Linear System Theory and Design

CHEN System and Signal Analysis, 2nd Ed.

COMER Digital Logic and State Machine Design, 3rd Ed.

COOPER AND MCGILLEM Probabilistic Methods of Signal and System Analysis, 2nd Ed.

FRANCO Electric Circuits Fundamentals

JONES Introduction to Optical Fiber Communication Systems

KREIN Elements of Power Electronics

KUO Digital Control Systems, 3rd Ed.

LATHI Modern Digital and Analog Communications Systems, 2nd Ed.

MCGILLEM AND COOPER Continuous and Discrete Signal and System Analysis, 3rd Ed.

MINER Lines and Electromagnetic Fields for Engineers

ROBERTS SPICE, 2nd Ed.

SANTINA Stubberud and Hostetter, Digital Control System Design, 2/E

SCHWARZ Electromagnetics for Engineers

SCHWARZ AND OLDHAM Electrical Engineering: An Introduction, 2nd Ed.

SEDRA AND SMITH Microelectronic Circuits, 4th Ed.

STEFANI, SAVANT, AND HOSTETTER Design of Feedback Control Systems, 3rd Ed.

VAN VALKENBURG Analog Filter Design

WARNER AND GRUNG Semiconductor Device Electronics

WOLOVICH Automatic Control Systems

YARIV Optical Electronics in Modern Communications, 5th Ed.

FOURTH EDITION



MICROELECTRONIC CIRCUITS

Adel S. Sedra
University of Toronto

Kenneth C. Smith
University of Toronto and Hong Kong
University of Science and Technology

New York Oxford
OXFORD UNIVERSITY PRESS
1998

Oxford University Press

Oxford New York
Athens Auckland Bangkok Bogota Bombay Buenos Aires
Calcutta Cape Town Dar es Salaam Delhi Florence Hong Kong
Istanbul Karachi Kuala Lumpur Madras Madrid Melbourne
Mexico City Nairobi Paris Singapore Taipei Tokyo Toronto Warsaw

and associated companies in

Berlin Ibadan

Copyright © 1998, 1991, 1987, 1982 by Oxford University Press, Inc.

Published by Oxford University Press, Inc.,
198 Madison Avenue, New York, New York, 10016
<http://www.oup-usa.org>

Oxford is a registered trademark of Oxford University Press

All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted, in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior permission of Oxford University Press.

Staff

Senior Acquiring Editor: *Bill Zobrist*
Editorial/Production/Design Manager: *Elyse Dubin*
Assistant Acquiring Editor: *Krysia Bebeck*
Production Coordinator: *John Bauco*
Editorial Assistant: *Jasmine Urmeneta*
Composition: *York Graphic Services*
Production Services: *York Production Services*
Director of Marketing: *Scott Burns*
Assistant Sales Manager: *Marcy Levine*
Advertising Manager: *David Walker*
Copywriter: *Leigh Ann Florek*
Cover Design: *Ed Berg Designs*
Cover Art Direction: *Linda Roppolo*
Manufacturing Director: *Ben Lee*
Manufacturing Controller: *Robin Meredith-Clement*

Library of Congress Cataloging-in-Publication Data

Sedra, Adel S.
Microelectronic circuits / Adel S. Sedra, Kenneth C. Smith. — 4th ed.
p. cm. — (Oxford series in electrical and computer engineering)
Includes bibliographical references and index.
ISBN 0-19-511663-1
1. Electronic circuits. 2. Integrated circuits. I. Smith,
Kenneth Carless. II. Title. III. Series.
TK7867.S39 1997 97-11254
621.381—dc21 CIP

9

Printed in the United States of America on acid-free paper

Cover Illustration: The chip shown is the ADXL-50 surface-micromachined accelerometer. For the first time, sensor and signal conditioning are combined on a single monolithic chip. In its earliest application, it was a key factor in the improved reliability and reduced cost of modern automotive airbag systems. Photo reprinted with permission of Analog Devices, Inc.



DETAILED TABLE OF CONTENTS

PREFACE v

Chapter 1 INTRODUCTION TO ELECTRONICS 1

- Introduction 1
- 1.1 Signals 2
- 1.2 Frequency Spectrum of Signals 3
- 1.3 Analog and Digital Signals 6
- 1.4 Amplifiers 9
- 1.5 Circuit Models for Amplifiers 19
- 1.6 Frequency Response of Amplifiers 28
- 1.7 The Digital Logic Inverter 39
- Summary 47
- Bibliography 48
- Problems 48

PART I DEVICES AND BASIC CIRCUITS 58

Chapter 2 OPERATIONAL AMPLIFIERS 60

- Introduction 60
- 2.1 The Op-Amp Terminals 61
- 2.2 The Ideal Op Amp 62
- 2.3 Analysis of Circuits Containing Ideal Op Amps—The Inverting Configuration 64
- 2.4 Other Applications of the Inverting Configuration 71
 - 2.4.1 The Inverting Configuration with General Impedances Z_1 and Z_2 71
 - 2.4.2 The Inverting Integrator 73
 - 2.4.3 The Op Amp Differentiator 78
 - 2.4.4 The Weighted Summer 80
- 2.5 The Noninverting Configuration 81
- 2.6 Examples of Op-Amp Circuits 85
- 2.7 Effect of Finite Open-Loop Gain and Bandwidth on Circuit Performance 92
- 2.8 Large-Signal Operation of Op Amps 97
- 2.9 DC Imperfections 101
- Summary 108
- Bibliography 109
- Problems 110

Chapter 3 DIODES 122

Introduction 122

- 3.1 The Ideal Diode 123
- 3.2 Terminal Characteristics of Junction Diodes 131
- 3.3 Physical Operation of Diodes 137
 - 3.3.1 Basic Semiconductor Concepts 138
 - 3.3.2 The pn Junction Under Open-Circuit Conditions 143
 - 3.3.3 The pn Junction Under Reverse-Bias Conditions 146
 - 3.3.4 The pn Junction in the Breakdown Region 149
 - 3.3.5 The pn Junction Under Forward-Bias Conditions 151
 - 3.3.6 Summary 155
- 3.4 Analysis of Diode Circuits 155
- 3.5 The Small-Signal Model and Its Application 163
- 3.6 Operation in the Reverse Breakdown Region—Zener Diodes 172
- 3.7 Rectifier Circuits 179
- 3.8 Limiting and Clamping Circuits 191
- 3.9 Special Diode Types 196
- 3.10 The SPICE Diode Model and Simulation Examples 199
 - Summary 206
 - Bibliography 206
 - Problems 207

Chapter 4 BIPOLAR JUNCTION TRANSISTORS (BJTs) 221

Introduction 221

- 4.1 Physical Structure and Modes of Operation 222
- 4.2 Operation of the nnp Transistor in the Active Mode 223
- 4.3 The pnp Transistor 232
- 4.4 Circuit Symbols and Conventions 234
- 4.5 Graphical Representation of Transistor Characteristics 238
- 4.6 Analysis of Transistor Circuits at DC 241
- 4.7 The Transistor as an Amplifier 253
- 4.8 Small-Signal Equivalent Circuit Models 259
- 4.9 Graphical Analysis 272
- 4.10 Biasing the BJT for Discrete-Circuit Design 276
- 4.11 Basic Single-Stage BJT Amplifier Configurations 282
- 4.12 The Transistor as a Switch—Cutoff and Saturation 295
- 4.13 A General Large-Signal Model for the BJT: The Ebers-Moll (EM) Model 303
- 4.14 The Basic BJT Logic Inverter 310
- 4.15 Complete Static Characteristics, Internal Capacitances, and Second-Order Effects 315
- 4.16 The SPICE BJT Model and Simulation Examples 326
 - Summary 331
 - Bibliography 332
 - Problems 333

Chapter 5 FIELD-EFFECT TRANSISTORS (FETs) 353

- Introduction 353
- 5.1 Structure and Physical Operation of the Enhancement-Type MOSFET 354
- 5.2 Current-Voltage Characteristics of the Enhancement MOSFET 366
- 5.3 The Depletion-Type MOSFET 376
- 5.4 MOSFET Circuits at DC 380
- 5.5 The MOSFET as an Amplifier 389
- 5.6 Biasing in MOS Amplifier Circuits 400
 - 5.6.1 Biasing of Discrete MOSFET Amplifiers 400
 - 5.6.2 Biasing in Integrated-Circuit MOS Amplifiers 402
- 5.7 Basic Configurations of Single-Stage IC MOS Amplifiers 408
 - 5.7.1 The CMOS Common-Source Amplifier 409
 - 5.7.2 The CMOS Common-Gate Amplifier 413
 - 5.7.3 The Common-Drain or Source-Follower Configuration 416
 - 5.7.4 All-NMOS Amplifier Stages 419
 - 5.7.5 A Final Remark 425
- 5.8 The CMOS Digital Logic Inverter 425
- 5.9 The MOSFET as an Analog Switch 436
- 5.10 The MOSFET Internal Capacitances and High-Frequency Model 441
- 5.11 The Junction Field-Effect Transistor (JFET) 447
- 5.12 Gallium Arsenide (GaAs) Devices—The MESFET 452
- 5.13 The SPICE MOSFET Model and Simulation Examples 458
 - Summary 464
 - Bibliography 464
 - Problems 466

PART II ANALOG CIRCUITS 484

Chapter 6 DIFFERENTIAL AND MULTISTAGE AMPLIFIERS 487

- Introduction 487
- 6.1 The BJT Differential Pair 487
- 6.2 Small-Signal Operation of the BJT Differential Amplifier 492
- 6.3 Other Nonideal Characteristics of the Differential Amplifier 504
- 6.4 Biasing in BJT Integrated Circuits 508
- 6.5 The BJT Differential Amplifier with Active Load 522
- 6.6 MOS Differential Amplifiers 527
- 6.7 BiCMOS Amplifiers 537
- 6.8 GaAs Amplifiers 542
- 6.9 Multistage Amplifiers 551
- 6.10 SPICE Simulation Example 558
 - Summary 563
 - Bibliography 564
 - Problems 564

Chapter 7 FREQUENCY RESPONSE 583

- Introduction 583
- 7.1 s-Domain Analysis: Poles, Zeros, and Bode Plots 584
- 7.2 The Amplifier Transfer Function 590
- 7.3 Low-Frequency Response of the Common-Source and Common-Emitter Amplifiers 602
- 7.4 High-Frequency Response of the Common-Source and Common-Emitter Amplifiers 610
- 7.5 The Common-Base, Common-Gate, and Cascode Configurations 619
- 7.6 Frequency Response of the Emitter and Source Followers 626
- 7.7 The Common-Collector Common-Emitter Cascade 630
- 7.8 Frequency Response of the Differential Amplifier 635
- 7.9 SPICE Simulation Examples 645
- Summary 649
- Bibliography 650
- Problems 650

Chapter 8 FEEDBACK 667

- Introduction 667
- 8.1 The General Feedback Structure 668
- 8.2 Some Properties of Negative Feedback 670
- 8.3 The Four Basic Feedback Topologies 675
- 8.4 The Series-Shunt Feedback Amplifier 679
- 8.5 The Series-Series Feedback Amplifier 688
- 8.6 The Shunt-Shunt and the Shunt-Series Feedback Amplifiers 696
- 8.7 Determining the Loop Gain 708
- 8.8 The Stability Problem 713
- 8.9 Effect of Feedback on the Amplifier Poles 715
- 8.10 Stability Study Using Bode Plots 725
- 8.11 Frequency Compensation 729
- 8.12 SPICE Simulation Examples 735
- Summary 740
- Bibliography 740
- Problems 741

Chapter 9 OUTPUT STAGES AND POWER AMPLIFIERS 751

- Introduction 751
- 9.1 Classification of Output Stages 752
- 9.2 Class A Output Stage 753
- 9.3 Class B Output Stage 758

9.4	Class AB Output Stage	764
9.5	Biasing the Class AB Circuit	767
9.6	Power BJTs	773
9.7	Variations on the Class AB Configuration	780
9.8	IC Power Amplifiers	785
9.9	MOS Power Transistors	792
9.10	SPICE Simulation Example	797
	Summary	802
	Bibliography	802
	Problems	803

Chapter 10 ANALOG INTEGRATED CIRCUITS 810

	Introduction	810
10.1	The 741 Op-Amp Circuit	811
10.2	DC Analysis of the 741	815
10.3	Small-Signal Analysis of the 741 Input Stage	822
10.4	Small-Signal Analysis of the 741 Second Stage	828
10.5	Analysis of the 741 Output Stage	830
10.6	Gain and Frequency Response of the 741	835
10.7	CMOS Op Amps	840
10.8	Alternative Configurations for CMOS and BiCMOS Op Amps	850
10.9	Data Converters—An Introduction	856
10.10	D/A Converter Circuits	860
10.11	A/D Converter Circuits	864
10.12	SPICE Simulation Example	870
	Summary	874
	Bibliography	875
	Problems	876

Chapter 11 FILTERS AND TUNED AMPLIFIERS 884

	Introduction	884
11.1	Filter Transmission, Types, and Specification	885
11.2	The Filter Transfer Function	889
11.3	Butterworth and Chebyshev Filters	892
11.4	First-Order and Second-Order Filter Functions	900
11.5	The Second-Order LCR Resonator	909
11.6	Second-Order Active Filters Based on Inductor Replacement	915
11.7	Second-Order Active Filters Based on the Two-Integrator-Loop Topology	923
11.8	Single-Amplifier Biquadratic Active Filters	929
11.9	Sensitivity	938

11.10	Switched-Capacitor Filters	941
11.11	Tuned Amplifiers	946
11.12	SPICE Simulation Examples	959
	Summary	965
	Bibliography	966
	Problems	967

Chapter 12 SIGNAL GENERATORS AND WAVEFORM-SHAPING CIRCUITS 973

	Introduction	973
12.1	Basic Principles of Sinusoidal Oscillators	974
12.2	Op Amp-RC Oscillator Circuits	980
12.3	LC and Crystal Oscillators	988
12.4	Bistable Multivibrators	994
12.5	Generation of Square and Triangular Waveforms Using Astable Multivibrators	1002
12.6	Generation of a Standardized Pulse—The Monostable Multivibrator	1007
12.7	Integrated-Circuit Timers	1009
12.8	Nonlinear Waveform-Shaping Circuits	1014
12.9	Precision Rectifier Circuits	1018
12.10	SPICE Simulation Examples	1026
	Summary	1030
	Bibliography	1030
	Problems	1031

PART III **DIGITAL CIRCUITS** 1040

Chapter 13 MOS DIGITAL CIRCUITS 1042

	Introduction	1042
13.1	Digital Circuit Design: An Overview	1043
	13.1.1 Digital IC Technologies and Logic-Circuit Families	1043
	13.1.2 Logic-Circuit Characterization	1045
	13.1.3 Styles for Digital System Design	1048
	13.1.4 Design Abstraction and Computer Aids	1048
13.2	Design and Performance Analysis of the CMOS Inverter	1049
13.3	CMOS Logic-Gate Circuits	1058
13.4	Pseudo-NMOS Logic Circuits	1070
13.5	Pass-Transistor Logic Circuits	1080
13.6	Dynamic Logic Circuits	1090
13.7	Latches and Flip-Flops	1097
13.8	Multivibrator Circuits	1106
13.9	Semiconductor Memories: Types and Architectures	1113

13.10	Random-Access Memory (RAM) Cells	1116
13.11	Sense Amplifiers and Address Decoders	1125
13.11.1	The Sense Amplifier	1125
13.11.2	The Row-Address Decoder	1131
13.11.3	The Column-Address Decoder	1133
13.12	Read-Only Memory (ROM)	1133
13.13	SPICE Simulation Example	1140
	Summary	1144
	Bibliography	1146
	Problems	1146

Chapter 14 BIPOLAR AND ADVANCED-TECHNOLOGY DIGITAL CIRCUITS 1158

	Introduction	1158
14.1	Dynamic Operation of the BJT Switch	1159
14.2	Early Forms of BJT Digital Circuits	1163
14.3	Transistor-Transistor Logic (TTL or T ² L)	1167
14.4	Characteristics of Standard TTL	1180
14.5	TTL Families with Improved Performance	1187
14.6	Emitter-Coupled Logic (ECL)	1195
14.7	BiCMOS Digital Circuits	1211
14.8	Gallium-Arsenide Digital Circuits	1216
14.9	SPICE Simulation Example	1224
	Summary	1230
	Bibliography	1231
	Problems	1232

APPENDIXES

A	VLSI FABRICATION TECHNOLOGY	A-1
B	TWO-PORT NETWORK PARAMETERS	B-1
C	AN INTRODUCTION TO SPICE	C-1
D	INPUT FILES FOR THE SPICE EXAMPLES	D-1
E	SOME USEFUL NETWORK THEOREMS	E-1
F	SINGLE-TIME-CONSTANT CIRCUITS	F-1
G	DETERMINING THE PARAMETER VALUES OF THE HYBRID-π BJT Model	G-1
H	STANDARD RESISTANCE VALUES AND UNIT PREFIXES	H-1
I	ANSWERS TO SELECTED PROBLEMS	I-1

	INDEX	IN-1
--	--------------	-------------