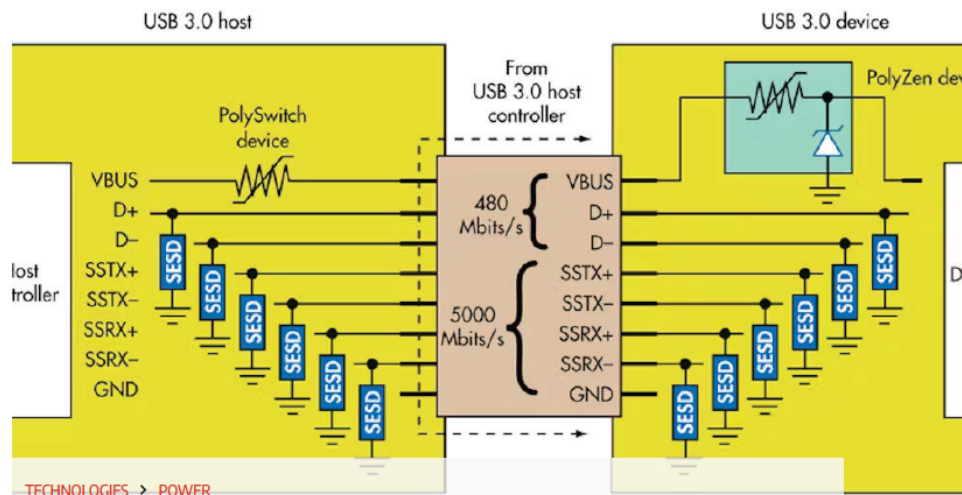


DigiKey
 Authorized Distributor

MAX17614 4.5V to 60V, 3A, Ideal Diode/Power Source Selector
 Full-featured adjustable protection

ANALOG DEVICES
 HEAD OF WHAT'S POSSIBLE™

[Learn more](#)


TECHNOLOGIES → POWER

Automotive Electronics Drive The Need For Circuit Protection

May 7, 2014

Circuit protection devices are becoming smaller and more sophisticated to meet safety and reliability requirements in automotive infotainment systems

Barry Brents



The electronic content in modern cars has increased tremendously thanks to the demand for in-car entertainment ("infotainment") systems and features, such as docking for smartphones, USB ports, and satellite radios. The latest cars also are expected to boast GPS navigation systems with mapping capabilities, interior and exterior LED lighting, and other sophisticated features.

Government requirements for safety features are adding impetus to the proliferation of in-vehicle electronics as well. For example, backup cameras **will be mandatory in new cars in 2018**. Meanwhile, state laws requiring hands-free calling while driving mean that cell-phone interfaces will become standard features.

ADVERTISEMENT

<https://www.electronicdesign.com/technologies/power/article/21799679/automotive-electronics-drive-the-need-for-circuit-protection>

LPDDR5 DRAM
 5G smartphones
 and AI


NEW

Cars Will Enlist
Thermal Infrared and
AI to Shield...

Smart Cable Module
Pushes the Limits of
PCIe Connectivity

Exploring Uncommon
Applications of
Isolation

MOST READ

Edge AI Video
Analytics Solution
Adopts PICMG Box ...

Lasers Plus MEMS
Mirrors Deliver
Programmable...

DigiKey
Authorized Distributor

ECX-31B Series
32.768 kHz
Tuning Fork
Crystal

3.2 x 1.5 mm 70 kΩ
ESR standard
±20 ppm tolerance

[Learn more](#)

ECS INC
INTERNATIONAL

Automotive-Grade
MEMS Pressure
Sensor Handles Gas...

SPONSORED

USB Type-C®
Standardization –
Where, When, and...

ADAS: The technology
driving automotive
safety forward

Frequently asked
questions and
answers for RS-485...



Download this article in .PDF format


This file type includes high resolution graphics and schematics when applicable.

USB Applications

USB 3.0 ports are now common in cars. In addition to overcurrent and overvoltage protection, sensitive electronics that use high-speed USB (and HDMI and other high-speed interfaces) require protection against electrostatic discharge (ESD). Three different types of circuit protection devices can help stave off these potentially damaging events.


A PolySwitch PPTC (polymeric positive temperature coefficient) device can be used for resettable protection in USB applications (*Fig. 1, left*). Placing the PPTC device on the VBUS port of a USB power source limits the current in the event of a short circuit. It also helps prevent overcurrent damage caused by a sudden short circuit downstream and helps achieve UL60950 compliance.

ADVERTISEMENT

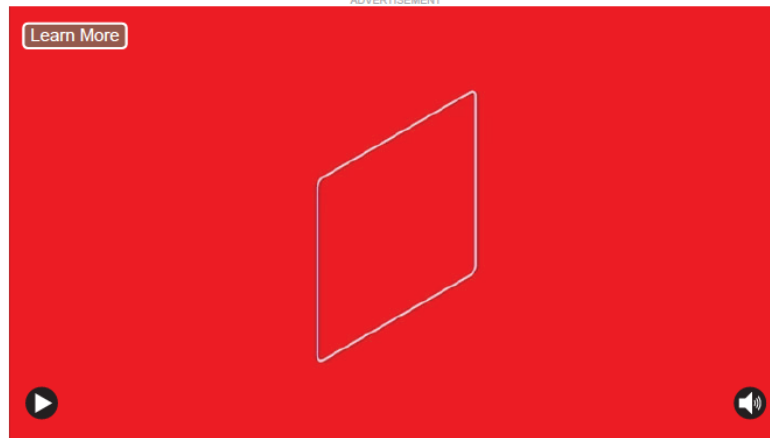

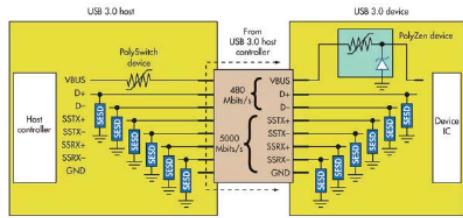1. USB 3.0 designs employ devices that protect against overcurrent (PPTC, left) and overvoltage (PolyZen, right) on the power ports and ESD (SESD devices) events on the data ports.

For overvoltage protection in USB 3.0 applications, the PolyZen device uses a hybrid approach (*Fig. 1, right*). It integrates a Zener diode and a PPTC device, which are thermally bonded. PolyZen parts can be



used inside USB ports to prevent an upstream regulator failure from putting out a high voltage that can damage components plugged into the USB port.

Finally, for ESD protection, circuit protection products such as silicon ESD (SESD) devices can be placed on the USB data lines. These ultra-compact (0402- and 0201- sized) devices have the low

capacitance that high-speed applications like USB 3.0 need.

12-V dc Systems

Power that feeds video monitors on the backs of seats, powered antennas, and other accessories needs short-circuit protection. It is very easy to short out power to the vehicle ground when installing equipment. Docking ports also have power outputs that need short-circuit protection.

ADVERTISEMENT

Traditionally, fuses have protected power inputs and outputs in 12-V dc systems. PolySwitch PPTCs offer a cost-effective, resettable alternative to fuses by helping to protect driver outputs from inadvertent short circuits or other load anomalies.

Video Outputs

Video outputs in car infotainment and other systems also need ESD protection. HDMI and other high-frequency outputs need low-capacitance ESD protection. When designing HDMI systems, using ESD protection devices that can operate at 3.4 GHz without affecting the signal integrity minimizes design headaches, increases system margin, and facilitates next-generation designs by eliminating the need for a full redesign of the ESD protection scheme down the road.

RF Outputs


RF outputs such as Bluetooth, GPS, and satellite radio antennas may need ESD protection as well. Protecting exposed communication interfaces from ESD and other voltage surges induced through the antenna and the instrument's wireless (RF) interface is a critical design issue.

A PolyZen device can help protect the power input to a Bluetooth module (*Fig. 2*). Also, Polymer ESD (PESD) devices can be used to help protect the antenna against ESD surges. PESD devices, like SESD devices, have the low capacitance needed for high-speed data transmission lines and RF data lines. They are available in compact surface-mount device (SMD) packages and can withstand numerous ESD strikes.

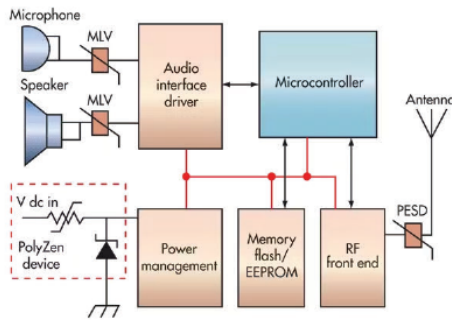2. Bluetooth modules can rely on PolyZen and PESD devices for circuit protection.

LED Lighting

Interior and exterior LEDs are increasingly being used in automotive designs. Although efficient and long lasting, LEDs are vulnerable to heat, ESD, and short-circuit anomalies that can lead to product



failure and potentially safety issues. Automotive manufacturers, therefore, use circuit protection for these lighting systems.

Most of the electrical energy supplied to an LED is changed into heat, not light. If not dealt with, the heat will reduce the LED's life and alter the quality of the light that is produced. A PolySwitch PPTC device can be used in series with the LED to provide overcurrent protection.

Additionally, this resettable device can provide overtemperature protection if it is thermally bonded to the metal core circuit board or LED heatsink. Problems can also occur if the LED driver's outputs are damaged or destroyed by being inadvertently shorted. If the driver circuit does not require input protection, PolySwitch PPTC devices can be used to help protect driver outputs.

ESD protection is also necessary if the LED does not have built-in protection. In this case, a PESD protection device placed in parallel with the LED can help protect against possible damage.


Many LED drivers are susceptible to destruction by improper dc voltage levels and polarity. Placing a PolyZen device on the input of the LED driver helps protect the driver from inadvertent exposure to overvoltage and reverse polarity events.

Conclusion


With the increase in car electronics designed for consumer entertainment and peace of mind comes the increasing potential for electronic failures, which, ironically, can result in the opposite effect: warranty repairs, safety issues, and overall customer dissatisfaction. That's why today's circuit protection devices go well beyond traditional fuses to help ensure reliability, performance, and safety in automotive electronics.

Barry Brents is a field application engineering manager with **TE Circuit Protection**, a business unit of **TE Connectivity**. A member of **IEEE** and former **U.S. Navy nuclear submarine officer**, he has been involved in the power and communications industries since 1989. He received his **BSEE** from **Texas Tech University**.

[CONTINUE READING](#)

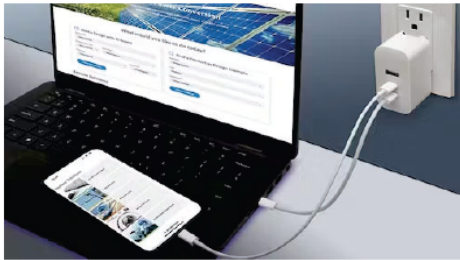

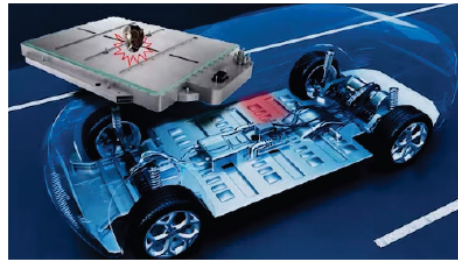Optimizing Single and Multi-Port USB PD 3.1 Power Supplies Using ZVS Flyback



EV Battery Collision Monitoring System Based on Touch-Sensing Tech

SPONSORED RECOMMENDATIONS



Podcast: The best battery on Earth is free and it is powering the new Blue Economy

Feb. 11, 2024



Podcast: HIRO pushes Europe to the edge with high performance microdata centers

Feb. 11, 2024



Podcast: The future of long-haul trucking is accelerating autonomously on a freeway near you

Feb. 11, 2024



Podcast: VideoRay drives safe, effective underwater exploration leveraging AI and today's newest technologies

Feb. 10, 2024

ElectronicDesign.

COMMENTS

Loading...

To join the conversation, and become an exclusive member of Electronic Design, create an account today!

[Join today!](#)

[I already have an account](#)

[Privacy & Cookie Policy](#)

© 2024 Endeavor Business Media, LLC. All rights reserved.

